
1- 64-bit Ladner Fischer adder:

Output and wave simulation

```
# At time
                            0, a =
                                                      0, b =
                                                                                0, cin = 0, sum =
                                                                                                                     0, cout = 0, {cout, sum} =
                                                                                                                                                                  25
At time
                        100000, a =
                                                     15, b =
                                                                               10, cin = 0, sum =
                                                                                                                    25, cout = 0, {cout, sum} =
# At time
                        20000, a =
                                                     15, b =
                                                                               10, cin = 1, sum =
                                                                                                                    26, cout = 0, {cout, sum} =
# At time
                        30000, a = 18446744073709551615, b =
                                                                                1, cin = 0, sum =
                                                                                                                     0, cout = 1, {cout, sum} = 18446744073709551616
# At time
                        40000, a = 18446744073709551615, b =
                                                                                1, cin = 1, sum =
                                                                                                                     1, cout = 1, {cout, sum} = 18446744073709551617
# At time
                        50000, a = 1311768467463790320, b = 18364758544493064720, cin = 0, sum = 1229782938247303424, cout = 1, {cout,sum} = 19676527011956855040
# At time
                        60000, a = 1311768467463790320, b = 18364758544493064720, cin = 1, sum = 1229782938247303425, cout = 1, {cout,sum} = 19676527011956855041
```

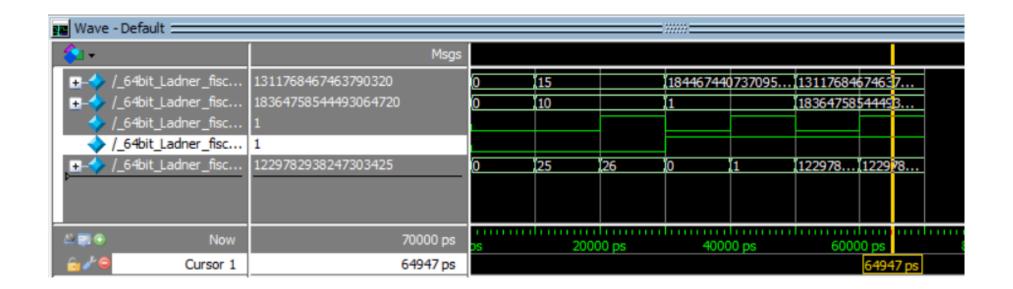

FPGA Utilization and Delay

			Table of Contents	4 4a	Propa	gation Delay					
Anal	ysis & Synthesis Resource Usage Summary		✓ Image: Variable of the property of the p			Input Port	Output Port	ŔŔ	RF	FR	FF
	Resource	Usage			1	a[4]	s[61]	35.522	37.046	35.712	37.236
1	Estimate of Logic utilization (ALMs needed)	102	> 🗀 Settings		2	a[3]	s[61]	35.502	37.026	35.653	37.177
2	5 ()		== Parallel Compilation		3	a[5]	s[61]	35.495	37.019	35.669	37.193
3	✓ Combinational ALUT usage for logic	171	■ Source Files Read		4	a[0]	s[61]	35.407	36.945	38.217	39.741
1	7 input functions	0	Resource Usage Summary		5	b[5]	s[61]	35.368	36.892	35.576	37.100
	6 input functions	32	Resource Utilization by Entity		6	b[4]	s[61]	35.356	36.880	35.504	37.028
2	· · · · · · · · · · · · · · · · · · ·		✓ ☑ Optimization Results		7	b[3]	s[61]	35.307	36.831	35.812	37.336
3	5 input functions	35	> Register Statistics		8	b[2]	s[61]	35.147	36.671	35.859	37.383
4	4 input functions	36	> Connectivity Checks		9	b[8]	s[61]	34.936	36.460	35.169	36.693
5	<=3 input functions	68	Elapsed Time Per Partition		10	a[8]	s[61]	34.904	36.428	35.022	36.546
4			Messages		11	a[2]	s[61]	34.811	36.335	35.425	36.949
5	Dedicated logic registers	0	Suppressed Messages		12	a[4]	s[63]	33.915	34.112	34.105	34.302
6			> in Fitter		13	a[3]	s[63]	33.895	34.092	34.046	34.243
7	I/O pins	194	> Assembler		14	a[5]	s[63]	33.888	34.085	34.062	34.259
8	Total DSP Blocks	0	✓ ImeQuest Timing Analyzer — — — — — — — — — — — — — — — — — —		15	a[4]	s[60]	33.818	34.091	34.008	34.281
9	Maximum fan-out node	_64bit_Lander_fischer_network:lfn carry_compine:a[0].cp1 G~0	Summary		16	a[3]	s[60]	33.798	34.071	33.949	34.222
			□ Parallel Compilation		17	a[5]	s[60]	33.791	34.064	33.965	34.238
10	Maximum fan-out	6	Clocks		18	a[0]	s[63]	33.764	33.968	36.610	36.807
11	Total fan-out	939	✓ 🧁 Slow 1100mV 85C Model		19	b[5]	s[63]	33.761	33.958	33.969	34.166
12	Average fan-out	1.68	Fmax Summary		20	b[4]	s[63]	33.749	33.946	33.897	34.094
			Timing Closure Recommendations		21	a[0]	s[60]	33.733	33.999	36.513	36.786
			Setup Summary		22	b[3]	s[63]	33.700	33.897	34.205	34.402
			Hold Summary		23	a[0]	cout	33.693			36.794
			Recovery Summary		24	b[5]	s[60]	33.664	33.937	33.872	34.145
			Removal Summary		25	b[4]	s[60]	33.652	33.925	33.800	34.073
			Minimum Pulse Width Summary		26	b[3]	s[60]	33.603	33.876	34.108	34.381
			✓ 🗁 Datasheet Report		27	a[4]	s[62]	33.573	33.720	33.763	33.910
			Propagation Delay		28	b[0]	s[61]	33.572	35.110	35.779	37.303
			Minimum Propagation Delay		29	a[3]	s[62]	33.553	33.700	33.704	33.851
critical noth dolay is 35,522			Metastability Report		30	a[5]	s[62]	33.546	33.693	33.720	33.867


critical path delay is 35.522

It is too large because it must be smaller than CLA adder and Ling adder but I don't know where is the problem

2- N-bit Ladner_Fischer adder:

Output and wave simulation

```
# At time
                                                                                0, cin = 0, sum =
                                                                                                                   0, cout = 0, {cout, sum} =
# At time
                                                     15, b =
                        10000, a =
                                                                               10, cin = 0, sum =
                                                                                                                    25, cout = 0, {cout, sum} =
# At time
                        20000, a =
                                                                               10, cin = 1, sum =
                                                                                                                   26, cout = 0, {cout, sum} =
# At time
                        30000, a = 18446744073709551615, b =
                                                                               1, cin = 0, sum =
                                                                                                                    0, cout = 1, {cout, sum} = 18446744073709551616
# At time
                        40000, a = 18446744073709551615, b =
                                                                               1, cin = 1, sum =
                                                                                                                    1, cout = 1, {cout, sum} = 18446744073709551617
# At time
                        50000, a = 1311768467463790320, b = 18364758544493064720, cin = 0, sum = 1229782938247303424, cout = 1, {cout, sum} = 19676527011956855040
# At time
                        60000, a = 1311768467463790320, b = 18364758544493064720, cin = 1, sum = 1229782938247303425, cout = 1, {cout, sum} = 19676527011956855041
```

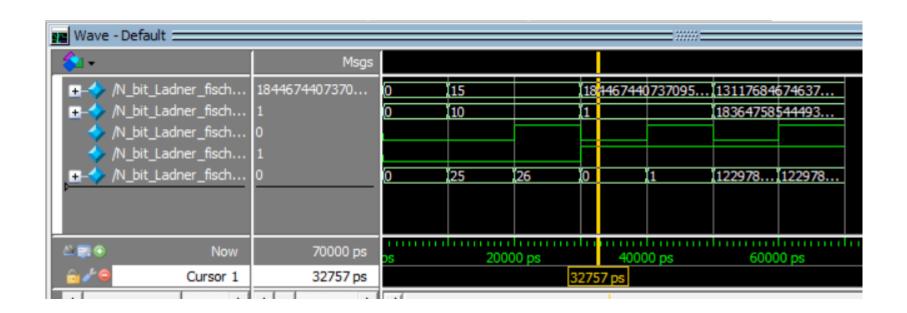

FPGA Utilization and Delay

